 


# CHAPTER 63

## Learning Objectives

- What is a FET
- Junction FET (JFET)
- Static Characteristics of a JFET
- JFET Drain Characteristic with  $V_{GS} = 0$
- Characteristics with External Bias
- Transfer Characteristic
- Small Signal JFET Parameters
- D.C. Biasing of a JFET
- DC Load Line
- Common Source JFET Amplifier
- JFET Amplifier Gains
- Advantages of FETs
- MOSFET or IGFET—DE MOSFET
- Schematic Symbols for a DEMOSFET
- Static Characteristics of a DEMOSFET
- Enhancement-only N-Channel MOSFET
- Biasing E-only MOSFET—FET Amplifiers
- FET Applications
- MOSFET Handling

## FIELD EFFECT TRANSISTORS



Field Effect Transistor as an Electronic Flute



### 63.1. What is a FET ?

The acronym 'FET' stands for **field effect transistor**. It is a three-terminal unipolar solid-state device in which current is controlled **by an electric field** as is done in vacuum tubes. Broadly speaking, there are two types of FETs :


- (a) junction field effect transistor (JFET)
- (b) metal-oxide semiconductor FET (MOSFET)

It is also called insulated-gate FET (IGFET). It may be further subdivided into :

- (i) depletion-enhancement MOSFET *i.e.* DEMOSFET
- (ii) enhancement-only MOSFET *i.e.* E-only MOSFET

Both of these can be either *P*-channel or *N*-channel devices.


The FET family tree is shown below :

 

### 63.2. Junction FET (JFET)
 
#### (a) Basic Construction

As shown in Fig. 63.1, it can be fabricated with either an *N*-channel or *P*-channel though *N*-channel is generally preferred. For fabricating an *N*-channel JFET, first a narrow bar of *N*-type semiconductor material is taken and then two *P*-type junctions are diffused on opposite sides of its middle part [Fig. 63.1 (a)]. These junctions form two *P-N* diodes or **gates** and the area between these gates is called **channel**. The two *P*-regions are internally connected and a single lead is brought out which is called **gate terminal**. Ohmic contacts (direct electrical connections) are made at the two ends of the bar—one lead is called **source terminal** *S* and the other **drain terminal** *D*. When potential difference is established between drain and source, current flows along the length of the 'bar' through the channel located between the two *P*-regions. The current consists of **only majority carriers** which, in the present case, are electrons. *P*-channel JFET is



similar in construction except that it uses  $P$ -type bar and two  $N$ -type junctions. The majority carriers are holes which flow through the channel located between the two  $N$ -regions or gates.

Following FET notation is worth remembering:

- 1. Source.** It is the terminal through which majority carriers enter the bar. Since carriers come from it, it is called the source.
- 2. Drain.** It is the terminal through which majority carriers *leave* the bar *i.e.* they are drained out from this terminal. The drain-to-source voltage  $V_{DS}$  drives the drain current  $I_D$ .
- 3. Gate.** These are two internally-connected heavily-doped impurity regions which form two  $P$ - $N$  junctions. The gate-source voltage  $V_{GS}$  reverse-biases the gates.
- 4. Channel.** It is the space between two gates through which majority carriers pass from source-to-drain when  $V_{DS}$  is applied.

 


Fig. 63.1

Schematic symbols for  $N$ -channel and  $P$ -channel JFET are shown in Fig. 63.1 (c). It must be kept in mind that **gate arrow always points to  $N$ -type material**.

#### (b) Theory of Operation

While discussing the theory of operation of a JFET, it should be kept in mind that

- 1.** Gates are always reversed-biased. Hence, gate current  $I_G$  is practically zero.
- 2.** The source terminal is always connected to that end of the drain supply which provides the necessary charge carriers. In an  $N$ -channel JFET, source terminal  $S$  is connected to the negative end of the drain voltage supply (for obtaining electrons). In a  $P$ -channel JFET,  $S$  is connected to the positive end of the drain voltage supply for getting holes which flow through the channel.

Let us now consider an  **$N$ -channel** JFET and discuss its working when either  $V_{GS}$  or  $V_{DS}$  or both are changed.

##### (i) When $V_{GS} = 0$ and $V_{DS} = 0$

In this case, drain current  $I_D = 0$ , because  $V_{DS} = 0$ . The depletion regions around the  $P$ - $N$  junctions are of equal thickness and symmetrical as shown in Fig. 63.2 (a)

##### (ii) When $V_{GS} = 0$ and $V_{DS}$ is increased from zero

For this purpose, the JFET is connected to the  $V_{DD}$  supply as shown in Fig. 63.2 (b). The electrons (which are the majority carriers) flow from  $S$  to  $D$  whereas conventional drain current  $I_D$  flows through the channel from  $D$  to  $S$ . Now, the gate-to-channel bias at any point along the channel is  $= |V_{DS}| + |V_{GS}|$  *i.e.* the numerical sum of the two voltages. In the present case, external bias  $V_{GS} = 0$ .



Hence gate-channel reverse bias is provided by  $V_{DS}$  alone. Since the value of  $V_{DS}$  keeps decreasing (due to progressive drop along the channel) as we go from  $D$  to  $S$ , the gate-channel bias also decreases accordingly. It has maximum value in the drain-gate region and minimum in the source-gate region. Hence, depletion regions penetrate more deeply into the channel in the drain-gate region than in the source-gate region. This explains why the depletion regions become wedge shaped when  $V_{DS}$  is applied [Fig. 63.2 (b)]

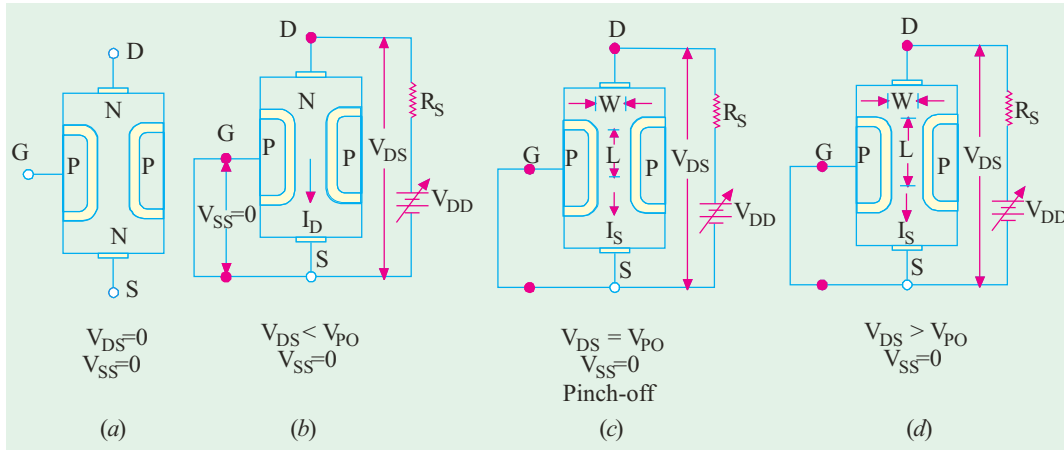


Fig. 63.2

As  $V_{DS}$  is gradually increased from zero,  $I_D$  increases proportionally as per Ohm's law. It is found that for small initial values of  $V_{DS}$ , the  $N$ -type channel material acts like a resistor of constant value. It is so because  $V_{DS}$  being small, the depletion regions are not large enough to have any significant effect on channel cross-section and, hence, its resistance. Consequently,  $I_D$  increases linearly as  $V_{DS}$  is increased from zero onwards (Fig. 63.5).

The ohmic relationship between  $V_{DS}$  and  $I_D$  continues till  $V_{DS}$  reaches a certain critical value called **pinch-off voltage**  $V_{PO}$  when drain current becomes constant at its maximum value called  $I_{DSS}$ . The SS in  $I_{DSS}$  indicates that the gate is shorted to source to make sure that  $V_{GS} = 0$ . This current is also known as **zero-gate-voltage drain current**. It is seen from Fig. 63.2(c) that under pinch-off conditions, separation between the depletion regions near the drain end reaches a minimum value  $W$ . It should, however, be carefully noted that **pinch-off does not mean 'current-off'**. In fact,  $I_D$  is maximum at pinch-off.

When  $V_{DS}$  is increased beyond  $V_{PO}$ ,  $I_D$  remains constant at its maximum value  $I_{DSS}$  upto a certain point. It is due to the fact that further increase in  $V_{DS}$  (beyond  $V_{PO}$ ) causes more of the channel on the source end to reach the minimum width as shown in Fig. 63.2 (d). It means that the channel width does not increase, instead its length  $L$  increases. As more of the channel reaches the minimum width, the resistance of the channel increases at the same rate at which  $V_{DS}$  increases. In other words, increase in  $V_{DS}$  is neutralized by increases in  $R_{DS}$ . Consequently,  $I_D = (V_{DS} / R_{DS})$  remains unchanged even though  $V_{DS}$  is increased. Ultimately, a certain value of  $V_{DS}$  (called  $V_{DSO}$ ) is reached when JFET breaks down and  $I_D$  increases to an excessive value as seen from drain characteristic of Fig. 63.5.

**(iii) When  $V_{DS} = 0$  and  $V_{GS}$  is decreased from zero**

In this case, as  $V_{GS}$  is made more and more negative, the gate reverse bias increases which increases the thickness of the depletion regions. As negative value of  $V_{GS}$  is increased, a stage comes when the two depletion regions touch each other as shown in Fig. 63.3. In this condition, the channel is said to be cut-off. This value of  $V_{GS}$  which cuts off the channel and

 


Fig. 63.3

hence the drain current is called  $V_{GS(off)}$ .\*

It may be noted that  $V_{GS(off)} = -V_{PO}$  or  $|V_{PO}| = |V_{GS(off)}|$ . As seen from Fig. 63.6 because  $V_{PO} = 4\text{ V}$ ,  $V_{GS(off)} = -4\text{ V}$ . Obviously, their absolute values are equal.

**(iv) When  $V_{GS}$  is negative and  $V_{DS}$  is increased**

As seen from Fig. 63.6, as  $V_{GS}$  is made more and more negative, values of  $V_P$  as well as breakdown voltage are decreased.

 


Fig. 63.4

**Summary.** Summarizing the above, we have that

(i) keeping  $V_{GS}$  at a fixed value (either zero or negative), as  $V_{DS}$  is increased,  $I_D$  initially increases till channel pinch-off when it becomes almost constant and finally increases excessively when JFET breaks down under high value of  $V_{DS}$ . As  $V_{GS}$  is kept fixed at progressively higher negative values, the values of  $V_P$  as well as breakdown voltage decrease.

(ii) keeping  $V_{DS}$  at a fixed value, as  $V_{GS}$  is made more and more negative,  $I_D$  decreases till it is reduced to zero for a certain value of  $V_{GS}$  called  $V_{GS(off)}$ .

Since gate voltage controls the drain current, JFET is called a **voltage-controlled** device. A P-channel JFET operates exactly in the same manner as an N-channel JFET except that current carriers are holes and polarities of both  $V_{DD}$  and  $V_{GS}$  are reversed.

Since only one type of majority carrier (either electrons or holes) is used in JFETs, they are called **unipolar devices** unlike bipolar junction transistors (BJTs) which use both electrons and holes as carriers.

### 63.3. Static Characteristics of a JFET

We will consider the following two characteristics:

**(i) drain characteristic**

It gives relation between  $I_D$  and  $V_{DS}$  for different values of  $V_{GS}$  (which is called running variable).

**(ii) transfer characteristic**

It gives relation between  $I_D$  and  $V_{GS}$  for different values of  $V_{DS}$ .

We will analyse these characteristics for an N-channel JFET connected in the common-source mode as shown in Fig. 63.4. We will first consider the drain characteristic when  $V_{GS} = 0$  and then when  $V_{GS}$  has any negative value upto  $V_{GS(off)}$ .

### 63.4. JFET Drain Characteristic With $V_{GS} = 0$

Such a characteristic is shown in Fig. 63.5 and has been already discussed briefly in Art. 63.2. It can be subdivided into following four regions :

#### 1. Ohmic Region OA

This part of the characteristic is linear indicating that for low values of  $V_{DS}$ , current varies directly with voltage following Ohm's Law. It means that JFET behaves **like an ordinary resistor** till

\* It has negative value for an N-channel JFET but a positive value for a P-channel JFET.



point A (called knee) is reached.

## 2. Curve AB

In this region,  $I_D$  increases at reverse square-law rate upto point B which is called **pinch-off point**. This progressive decrease in the rate of increase of  $I_D$  is caused by the square law increase in the depletion region at each gate upto point B where the two regions are closest without touching each other. The drain-to-source voltage  $V_{DS}$  corresponding to point B is called **pinch-off voltage  $V_p^*$** . But it is essential to remember that “pinch-off” does not mean “current-off”.

## 3. Pinch-off Region BC

It is also known as **saturation region** or ‘**amplified**’ region. Here, JFET operates as a constant-current device because  $I_D$  is relatively independent of  $V_{DS}$ . It is due to the fact that as  $V_{DS}$  increases, channel resistance also increases proportionally thereby keeping  $I_D$  practically constant at  $I_{DSS}$ . It should also be noted that the reverse bias required by the gate-channel junction is supplied entirely by the voltage drop across the channel resistance due to flow of  $I_{DSS}$  and none by external bias because  $V_{GS} = 0$ .

Drain current in this region is given by Shockley's equation

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2 = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

It is the normal operating region of the JFET when used as an amplifier.

## 4. Breakdown Region

If  $V_{DS}$  is increased beyond its value corresponding to point C (called avalanche breakdown voltage), JFET enters the breakdown region where  $I_D$  increases to an excessive value. This happens because the reverse-biased gate-channel P-N junction undergoes avalanche breakdown when small changes in  $V_{DS}$  produce very large changes in  $I_D$ .

It is interesting to note that increasing values of  $V_{DS}$  make a JFET behave first as a resistor (ohmic region), then as a constant-current source (pinch-off region) and finally, as a constant-voltage source (breakdown region).

## 63.5. JFET Characteristics With External Bias

Fig. 63.6 shows a family of  $I_D$  versus  $V_{DS}$  curves for different values of  $V_{GS}$ . It is seen that as the negative gate bias voltage is increased

(i) pinch off voltage is reached at a lower value of  $I_D$  than when  $V_{GS} = 0$ .

(ii) value of  $V_{DS}$  for breakdown is decreased.

When an external bias of, say,  $-1V$  is applied between the gate and source, the P-N junctions become reverse-biased even when  $I_D = 0$ . Hence,

 


Fig. 63.5

 


Fig. 63.6

\* It is numerically equal to  $V_{GS(off)}$  i.e.  $V_p = -V_{GS(off)}$

the depletion regions are already formed which penetrate the channel to a certain extent.

The amount of reverse bias required to be produced by  $I_D$  would, obviously, be decreased by 1V. In other words, a smaller voltage drop along the channel (*i.e.* smaller than when  $V_{GS} = 0$ ) will increase the depletion regions to the point where they will pinch off the current. Consequently,  $V_P$  is reached at a lower  $I_D$  value than when  $V_{GS} = 0$ .

Now, let us see why value of  $V_{DS}$  for breakdown is decreased as the negative gate bias voltage is increased. It is simply due to the fact that  $V_{GS}$  keeps adding to the reverse bias at the junction produced by current flow.

It is seen that with  $V_{GS} = 0$ ,  $I_D$  saturates at  $I_{DSS}$  and the characteristic shows  $V_P = 4V$ . When an external bias of  $-1V$  is applied, gate-channel junctions still require  $-4V$  to achieve pinch-off (remember,  $V_{GS} = -V_P$ ). It means that a 3V drop is now required along the channel instead of the previous 4V. Obviously, this 3V drop can be achieved with a lower value of  $I_D$ . Similarly, when  $V_{GS}$  is  $-2V$  and  $-3V$ , pinch-off is achieved with 2V and 1V respectively along the channel.

These drops of 2V and 1V are obtained with further-reduced values of  $I_D$ . As seen, when  $V_{GS} = -4V$  (*i.e.* numerically equal to  $V_P$ ), no channel drop is required. Hence,  $I_D$  is zero.

In general,  $V_P = V_{DS(P)} - V_{GS}$  where  $V_{DS(P)}$  is the pinch-off value of  $V_{DS}$  for a given value of  $V_{GS}$ .

### 63.6. Transfer Characteristic

It is a plot of  $I_D$  versus  $V_{GS}$  for a constant value of  $V_{DS}$  and is shown in Fig. 63.7. It is similar to the transconductance characteristics of a vacuum tube or a transistor. It is seen that when  $V_{GS} = 0$ ,  $I_D = I_{DSS}$  and when  $I_D = 0$ ,  $V_{GS} = V_P$ . The transfer characteristic approximately follows the equation.

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

The above equation can be written as

$$V_{GS} = V_{GS(off)} \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

This characteristic can be obtained from the drain characteristics by reading off  $V_{GS}$  and  $I_{DSS}$  values for different values of  $V_{DS}$ .


### 63.7. Small Signal JFET Parameters

The various parameters of a JFET can be obtained from its two characteristics. The main parameters of a JFET when connected in common-source mode are as under :

#### (i) AC Drain Resistance, $r_d$

It is the ac resistance between drain and source terminals when JFET is operating **in the pinch-off region**. It is given by

$$r_d = \frac{\text{change in } V_{DS}}{\text{change in } I_D} \text{ at } V_{GS} \text{ constant or } r_d = \frac{\Delta V_{DS}}{\Delta I_D} \bigg|_{V_{GS}}$$

 

This micrograph shows a mock field effect transistor with a layer of crystalline strontium titanate instead of silicon dioxide as the gate electrode.

 


Fig. 63.7



An alternative name is **dynamic drain resistance**. It is given by the slope of the drain characteristic in the pinch-off region. It is sometimes written as  $r_{ds}$  emphasizing the fact that it is the resistance from drain to source. Since  $r_d$  is usually the output resistance of a JFET, it may also be expressed as an output admittance  $y_{os}$ . Obviously,  $y_{os} = 1/r_d$ . It has a very high value.

### (ii) Transconductance, $g_m$

It is simply the slope of transfer characteristic.

$$g_m = \frac{\text{change in } I_D}{\text{change in } V_{GS}} \text{ at } V_{DS} \text{ constant or } g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS}}$$

Its unit is Siemens (S) earlier called **mho**. It is also called **forward transconductance ( $g_{fs}$ )** or **forward transadmittance  $y_{fs}$** .

The transconductance measured at  $I_{DSS}$  is written as  $g_{mo}$ .

### Mathematical Expression for $g_m$

The Shockley equation\* is  $I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$

Differentiating both sides, we have

$$\frac{dI_D}{dV_{GS}} = 2I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right) \left( -\frac{1}{V_P} \right) \text{ or } g_m = -\frac{2I_{DSS}}{V_P} \left( 1 - \frac{V_{GS}}{V_P} \right)$$

$$\text{When } V_{GS} = 0, \quad g_m = g_{mo} \quad \therefore \quad g_{mo} = -\frac{2I_{DSS}}{V_P}$$

$$\text{From the above two equations, we have } g_m = g_{mo} \left( 1 - \frac{V_{GS}}{V_P} \right) = g_{mo} \sqrt{\frac{I_D}{I_{DSS}}}$$

### (iii) Amplification Factor, $\mu$

It is given by  $\mu = \frac{\text{change in } V_{DS}}{\text{change in } V_{GS}} \text{ at } I_D \text{ constant or } \mu = \left. \frac{\Delta V_{DS}}{\Delta V_{GS}} \right|_{I_D}$

It can be proved from above that

$$\mu = g_m \times r_d = g_{fs} \times r_d$$

### (iv) DC Drain Resistance, $R_{DS}$

It is also called the static or ohmic resistance of the channel. It is given by

$$R_{DS} = \frac{V_{DS}}{I_D}$$

**Example 63.1.** For an N-channel JFET,  $I_{DSS} = 8.7 \text{ mA}$ ,  $V_P = -3 \text{ V}$ ,  $V_{GS} = -1 \text{ V}$ . Find the values of (i)  $I_D$  (ii)  $g_{mo}$  (iii)  $g_m$  (Basic Electronics, Bombay Univ., 1985)

$$\text{Solution. (i) } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 8.7 \left( 1 - \frac{-1 \text{ V}}{-3 \text{ V}} \right)^2 = 3.87 \text{ A}$$

$$\text{(ii) } g_{mo} = \frac{-2I_{DSS}}{V_P} = \frac{-2 \times 8.7}{-3} = 5.8 \text{ mS}$$

$$\text{(iii) } g_m = g_{mo} \left( 1 - \frac{V_{GS}}{V_P} \right) = 5.8 \left( 1 - \frac{-1}{-3} \right) = 3.87 \text{ mS}$$

\* Because of the squared term in the equation, JFET and MOSFET are referred to as square-law devices.





### 63.8. DC Biasing of a JFET

A JFET may be biased by using either

1. a separate power source  $V_{GG}$  as shown in Fig. 63.8 (a),
2. some form of self-bias as shown in Fig. 63.8 (b),
3. source bias as in Fig. 63.8 (c),
4. voltage divider bias as in Fig. 63.8 (d).

 


Fig. 63.8

The circuit of Fig. 63.8 (b) is called self-bias circuit because the  $V_{GS}$  bias is obtained from the flow of JFET's own drawn current  $I_D$  through  $R_S$ .

$$\therefore V_S = I_D R_S \quad \text{and} \quad V_{GS} = -I_D R_S$$

The gate is kept at this much negative potential with respect to the ground.

The addition of  $R_G$  in Fig. 63.8 (b), does not upset this dc bias for the simple reason that no gate current flows through it (the gate leakage current is almost zero). Hence, gate is essentially at **dc ground**. Without  $R_G$ , gate would be kept 'floating' which could collect charge and ultimately cut-off the JFET.

The resistance  $R_G$  additionally serves the purpose of avoiding short-circuiting of the ac input voltage,  $v_{in}$ . Moreover, in case leakage current is not totally negligible,  $R_G$  would provide it an escape route. Otherwise, the leakage current would build up static charge (voltage) at the gate which could change the bias or even destroy the JFET.

Fig. 63.8 (c) shows the *source bias* circuit which employs a self-bias resistor  $R_S$  to obtain  $V_{GS}$ . Here,  $V_{SS} = I_D R_S + V_{GS}$  or  $V_{GS} = V_{SS} - I_D R_S$ .

Fig. 63.8 (d) shows the familiar voltage divider bias. In this case,  $V_2 = V_{GS} + I_D R_S$  or  $V_{GS} = V_2 - I_D R_S$

$$\text{Since, } V_2 = V_{DD} \frac{R_2}{R_1 + R_2} \quad \therefore V_{GS} = V_{DD} \frac{R_2}{R_1 + R_2} - I_D R_S$$

**Example 63.2 .** Find the values of  $V_{DS}$  and  $V_{GS}$  in Fig. 63.9 for  $I_D = 4 \text{ mA}$ .

(Applied Electronics-I, Punjab Univ. 1992)

$$\begin{aligned} \text{Solution.} \quad V_S &= I_D R_S = 4 \times 10^{-3} \times 500 = 2.0 \text{ V} \\ V_D &= V_{DD} - I_D R_L = 12 - 4 \times 1.5 = 6 \text{ V} \\ \therefore V_{DS} &= V_D - V_S = 6 - 2 = 4 \text{ V} \\ \text{Since } V_G &= 0, V_{GS} = V_G - V_S = 0 - 2.0 = -2.0 \text{ V} \end{aligned}$$

### 63.9. DC Load Line

The dc load line for a JFET can be easily drawn by remembering the following two points :

(i) At  $I_D = 0, V_{DS} = V_{DD}$

(ii) At  $V_{DS} = 0, I_D = \frac{V_{DD}}{R_L}$



The  $Q$ -point is generally situated at the middle point of the load line (for class-A operation) so that

$$V_{DSQ} = \frac{1}{2} V_{DD}$$

$$\text{Also, } I_{DSQ} = \frac{\frac{1}{2} V_{DD}}{R_s + R_L}$$

**Example 63.3.** For the circuit of Fig. 63.11, find the values of  $V_{DSQ}$  and  $V_{GS}$  assuming centrally-located  $Q$ -point and zero gate current.

 


Fig. 63.10

**Solution.** Since  $I_G = 0$ , dc circuit is not disturbed.

$$V_{DS} = \frac{1}{2} V_{DD} = \frac{12}{2} = 6V$$

The balance of 6 V drops across series combination of  $R_L$  and  $R_S$ .

$$\therefore I_D = \frac{6}{150 + 450} = 10 \text{ mA}$$

$$\therefore V_{GS} = -I_D R_S = -10 \times 150 = -1.5 \text{ V}$$

It is obvious that gate is 1.5 V negative with respect to the source which is the common point. Incidentally, in common source connection of a JFET, **gate is the most negative point in the entire circuit.**

**Example 63.4.** What values of  $R_S$  and  $R_L$  are required for the circuit of Fig. 63.12 for setting up an approximate mid-point bias? The JFET parameters are :  $I_{DSS} = 16 \text{ mA}$ ,  $V_{GS(off)} = -8 \text{ V}$  and  $V_D = \frac{1}{2} V_{DD}$ .

**Solution.** It should be noted that as found from Shockley's equation, for mid-point bias,  $I_D \cong I_{DSS}/2$  and  $V_{GS} = V_{GS(off)}/4$ . Hence, for mid-point bias

$$I_D \cong 16/2 = 8 \text{ mA}$$

$$V_{GS} = \frac{1}{4} V_{GS(off)} = -\frac{8}{4} = -2 \text{ V}$$

 


Fig. 63.9

 


Fig. 63.11

 


Fig. 63.12

$$R_S = \frac{V_{GS}}{I_D} = \frac{2 \text{ V}}{8 \text{ mA}} = \mathbf{250 \, \Omega}$$

$$\text{Now, } V_D = V_{DD} - I_D R_L, R_L = \frac{V_{DD} - V_D}{I_D} = \frac{16 - 8}{8 \text{ mA}} = \mathbf{1000 \, \Omega}$$

**Example 63.5.** Determine the quiescent value of  $V_{GS}$ ,  $I_D$  and  $V_{DS}$  for the JFET circuit of Fig. 63.13 given that  $I_{DSS} = 10 \text{ mA}$ ,  $R_S = 5 \text{ K}$  and  $V_P = -5 \text{ V}$ .

(Electronic Devices & Circuits, Pune Univ. 1991)

 


Fig. 63.13

**Solution.** Since  $I_S \cong I_D$ ,  $V_{GS} = -I_D R_S = -5000 I_D$

$$\text{Now, } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \times 10^{-3} \left( 1 - \frac{V_{GS}}{-5} \right)^2$$

$$= 10 \times 10^{-3} (1 + 0.2 V_{GS})^2$$

Substituting this value in the above equation, we get

$$V_{GS} = -5000(10 \times 10^{-3}) (1 + 0.2 V_{GS})$$

Expanding and rearranging the above, we have

$$2V_{GS}^2 + 21V_{GS} + 50 = 0$$

$$\therefore V_{GS} = -3.65 \text{ V} \quad \text{or} \quad -6.85 \text{ V}$$

Rejecting the higher value because it is more than  $V_P$ , we have  $V_{GS} = \mathbf{-3.65 \text{ V}}$

$$\therefore -3.65 = -5000 I_D \quad \therefore I_D = \mathbf{0.73 \text{ mA}}$$

$$V_D = V_{DD} - I_D R_L = 12 - 0.73 \times 2 = \mathbf{1.54 \text{ V}}$$

$$V_S = I_D R_S = 0.73 \times 5 = 3.65 \text{ V} \quad \therefore V_{DS} = V_D - V_S = 10.54 - 3.65 = \mathbf{6.89 \text{ V}}$$

### 63.10. Common Source JFET Amplifier

A simple circuit for such an amplifier is shown in Fig. 63.14. Here,  $R_G$  serves the purpose of providing leakage path to the gate current,  $R_S$  develops gate bias,  $C_3$  provides ac ground to the input signal and  $R_L$  acts as drain load.

#### Working

When **negative-going** signal is applied to the input

1. gate **bias is increased**,
2. depletion regions are **widened**,
3. channel resistance is **increased**,
4.  $I_D$  is **decreased**,
5. drop across  $R_L$  is **decreased**,
6. Consequently, a **positive-going** signal becomes available at the output through  $C_2$  in Fig. 63.14.

When **positive-going signal** is applied at the input, then in a similar way, a **negative-going** signal becomes available at the output.

It is seen that there is a **phase inversion** between the input signal at the gate and output signal at the drain.

 


Fig. 63.14



## 63.11. JFET Amplifier Gains

We will now find the expressions for voltage gain, input resistance, output resistance and input capacitance of a JFET amplifier when connected in different modes. The different capacitance due to  $P-N$  junction and channel are shown in Fig. 63.15

## (a) Common Source JFET Amplifier (Fig. 63.16)

(i) Input Resistance  $r_i = R_G \parallel R_{GS}$ 

In an ideal JFET,  $R_{GS}$  is infinite because  $I_G = 0$ . In an actual device, however,  $R_{GS}$  is not actually infinite but extremely high (100 M or so) as compared to  $R_G$ . Hence,  $r_i \cong R_G$ .

(ii) Output Resistance  $r_o' = r_d \parallel R_L \cong R_L$  — if  $r_d \gg R_L$ 

## (iii) Voltage Gain

$$V_o = i_d \times r_d \parallel R_L \quad \text{Now, } i_d = -g_m \times v_i$$

$$\therefore V_o = -g_m V_i \times (r_d \parallel R_L)$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{-g_m V_i \times (r_d \parallel R_L)}{V_i} = \frac{-g_m r_d R_L}{r_d + R_L} = \frac{-\mu R_L}{r_d + R_L}$$

$$\text{Also, } A_v = -g_{fs} \times (r_d \parallel R_L)$$

 


Fig. 63.15

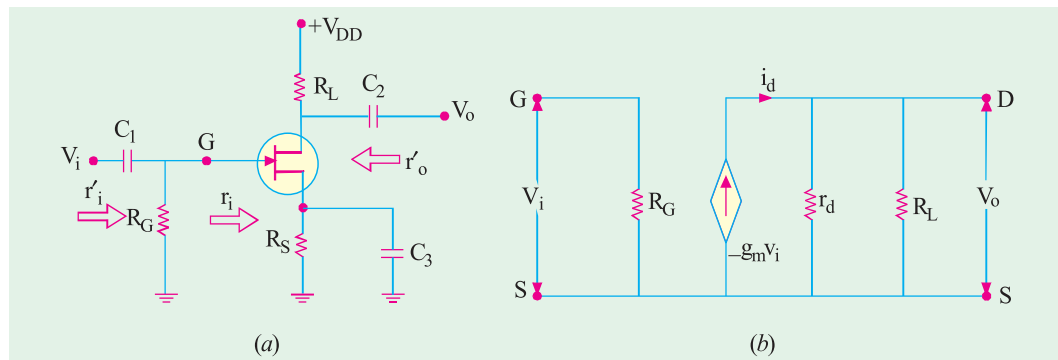


Fig. 63.16

## (iv) Input Capacitance

The input capacitance is  $C_{gs}$  which is increased because of Miller effect.

$$\therefore C_i = C_{gs} + (1 - A_v) C_{gd}$$

It is the large value of  $C_{gd}$  which is harmful in high-frequency work.

**Example 63.6.** The common-source amplifier of Fig. 63.16 (a) has  $r_d = 100 \text{ K}$ ,  $R_L = 10 \text{ K}$ ,  $g_m = 3000 \mu\text{S}$ ,  $C_{gs} = 3 \text{ pF}$  and  $C_{gd} = 1.5 \text{ pF}$ . Compute its (i)  $A_v$  and (ii)  $C_i$ .

$$\begin{aligned} \text{Solution. (i)} \quad A_v &= \frac{-g_m r_d R_L}{r_d + R_L} \\ &= \frac{-3000 \times 10^{-6} \times 100 \times 10^3 \times 10 \times 10^3}{(100 \times 10^3) + (10 \times 10^3)} = -27.3 \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad C_i &= C_{gs} + (1 - A_v) C_{gd} \\ &= 3 + (1 + 27.3) \times 1.5 = 45.5 \text{ pF.} \end{aligned}$$

 


Fig. 63.17

**Example 63.7.** The JFET shown in Fig. 63.17 has  $g_m = 3000 \mu S$  and  $r_{ds} = 100 K$ . Calculate the voltage gain of the CS amplifier circuit. (Basic Electronics, Bombay Univ. 1992)

**Solution.** As seen from Art. 63.11 (a)

$$\begin{aligned} A_v &= -g_m \times (r_{ds} \parallel r_L) \\ \text{Now, } r_L &= 10 K \parallel 10 K = 5 K \\ \therefore r_{ds} \parallel r_L &= 100 K \parallel 5 K = 4.76 K \\ \therefore A_v &= -3000 \times 10^{-6} \times 4.76 = -14.3 \end{aligned}$$

**(b) Common Drain JFET Amplifier**

In the common-drain circuit (also called source follower), the load resistance is in series with the source terminal. There is no drain resistor as shown in Fig. 63.18 (a). The input signal is applied to the gate through the capacitor  $C_1$  and the output is taken out from the source via  $C_2$ . The common-drain equivalent circuit is shown in Fig. 63.18 (b). The current generator is  $g_m V_{gs}$  where  $V_{gs} = (V_i - V_o)$ . Moreover,  $R_G = R_1 \parallel R_2$ .

**(i) Voltage Gain**

$$\begin{aligned} V_o &= i_d \times (r_d \parallel R_L). & \text{Since, } i_d &= g_m V_{gs} = g_m (V_i - V_o), \\ \therefore V_o &= g_m (V_i - V_o) \times (r_d \parallel R_L) = g_m (V_i - V_o), \frac{r_d R_L}{r_d + R_L} \end{aligned}$$

 


Fig. 63.18

Solving for  $V_o$ , we get

$$V_o = g_m V_i \frac{r_d R_L}{r_d + R_L + g_m r_d R_L} \quad \dots(i)$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{r_d R_L}{r_d + R_L + g_m r_d R_L} \cong 1 \quad \text{— if } g_m r_d R_L \gg (r_d + R_L)$$

**(ii) Input Resistance**

$$r'_{in} = R_1 \parallel R_2$$

— for circuit of Fig. 63.18 (a) only.

**(iii) Output Resistance**

In Eq. (i) above,  $g_m V_i$  is a current which is directly proportional to  $V_i$  and  $(r_d R_L) / (r_d + R_L + g_m r_d R_L)$  is a resistance,  $r'_o$ .

$$\begin{aligned} \therefore r'_o &= \frac{r_d R_L}{r_d + R_L + g_m r_d R_L} = \frac{[r_d / (1 + g_m r_d)] \times R_L}{[r_d / (1 + g_m r_d)] + R_L} \\ &= \frac{r_d}{1 + g_m r_d} \parallel R_L \cong \frac{1}{g_m} \parallel R_L \end{aligned}$$

The above result helps us to draw the modified equivalent circuit of Fig. 63.19 for the common-drain amplifier.

 


Fig. 63.19

**Example 63.8.** The common-drain circuit of Fig. 63.18 (a) uses a JFET having the following parameters :

$$r_d = 100 \text{ K}, \quad g_m = 3000 \text{ } \mu\text{S} \text{ and } R_L = 10 \text{ K}$$

Calculate (i)  $A_v$  and (ii)  $r'_o$ .

**Solution.** (i)  $A_v = g_m \frac{r_d R_L}{r_d + R_L + g_m r_d R_L}$

$$= 3000 \times 10^{-6} \frac{100 \times 10^3 \times 10 \times 10^3}{(100 \times 10^3) + (10 \times 10^3) + (3000 \times 10^{-6} \times 100 \times 10^3 \times 10 \times 10^3)} = 0.965$$

(ii)  $r'_o = R_L \parallel \frac{r_d}{1 + g_m r_d}$

Now,  $\frac{r_d}{1 + g_m r_d} = \frac{100 \times 10^3}{1 + 3000 \times 10^{-6} \times 100 \times 10^3} = 330 \text{ } \Omega$

$$r'_o = 10 \text{ K} \parallel 330 \text{ } \Omega \approx 320 \text{ } \Omega$$

### (c) Common Gate JFET Amplifier

In this amplifier configuration, input signal is applied to the source terminal and output is taken from the drain as shown in Fig. 63.20 (a). The gate is grounded,  $R_L$  is in series with drain and a source resistance  $R_S$  is included in the circuit across which  $V_i$  is dropped.

The ac equivalent circuit is shown in Fig. 63.20 (b) where current source is connected between the

 


Fig. 63.20

**drain and the source terminals as always.** However, since source and drain are the input and output terminals respectively,  $(g_m V_{gs})$  appears between the input and the output.

#### (i) Voltage Gain

$$V_o = i_d \times (r_d \parallel R_L) = i_d \cdot \frac{r_d R_L}{r_d + R_L}$$

Now,  $i_d = g_m V_{gs} = g_m V_i$   $\therefore V_o = g_m V_i \cdot \frac{r_d R_L}{r_d + R_L}$   $\therefore A_v = \frac{V_o}{V_i} = \frac{g_m r_d R_L}{r_d + R_L}$

It is the same as the gain for a common source amplifier except that it is a positive quantity. It means that  $V_o$  and  $V_i$  are in phase as shown in Fig. 63.20 (a).

#### (ii) Input Resistance

If we ignore current through  $R_S$ , then as seen from the ac equivalent circuit of Fig. 63.20 (b), input current is  $i_d$ . Now,  $i_d = g_m V_{gs} = g_m V_i$ .

The input resistance of the device i.e. JFET is  $r_i = \frac{V_i}{i_d} = \frac{V_i}{g_m V_i} = \frac{1}{g_m}$



The input resistance of the circuit is  $r_i' = r_i \parallel R_S = \frac{1}{g_m} \parallel R_S$

Actually speaking,  $r_d$  and  $R_L$  are also involved in  $r_i'$  but their effect is negligible.

### (iii) Output Resistance

As seen from the equivalent circuit of Fig. 63.20 (b),  $r_o' = r_d \parallel R_L$ .

Here, only input capacitance of importance is  $C_{gs}$ . Hence, this circuit has low input capacitance as compared to common-source circuit where input capacitance is increased due to Miller effect.\*

## 63.12. Advantages of FETs

FETs combine the many advantages of both BJTs and vacuum tubes. Some of their main advantages are :

1. high input impedance,
2. small size,
3. ruggedness,
4. long life,
5. high frequency response,
6. low noise,
7. negative temperature coefficient, hence better thermal stability,
8. high power gain,
9. a high immunity to radiations,
10. no offset voltage when used as a switch (or chopper),
11. square law characteristics.

The only disadvantages are :

1. small gain-bandwidth product,
2. greater susceptibility to damage in handling them.

### Tutorial Problems No. 63.1

1. For a particular *N*-channel JFET,  $V_{GS(off)} = -4$  V. What would be the value of  $I_D$  when  $V_{GS} = -6$  V? [zero]
2. For the *N*-channel JFET shown in Fig. 63.21,  $V_P = 8$  V and  $I_{DSS} = 12$  mA. What would be the value of (i)  $V_{DS}$  at which pinch-off begins and (ii) value of  $I_D$  when  $V_{DS}$  is above pinch-off but below the breakdown voltage? [3V ; 12 mA]
3. The data sheet of a JFET indicates that it has  $I_{DSS} = 15$  mA and  $V_{GS(off)} = -5$  V. Calculate the value of  $I_D$  when  $V_{GS}$  is (i) 0, (ii)  $-1$  V and (iii)  $-4$  V. [(i) 15 mA (ii) 9.6 mA (iii) 0.6 mA]
4. The data sheet of a JEET gives the following information.  
 $I_{DSS} = 20$  mA,  $V_{GS(off)} = -8$  V.  
 $g_{mo} = 4000$   $\mu$ S.  
 Calculate the value of  $I_D$  and  $g_m$  for  $V_{GS} = -4$  V. [5 mA ; 2000  $\mu$ S]
5. For a JEET,  $I_{DSS} = 5$  mA and  $g_{mo} = 4000$   $\mu$ S.  
 Calculate (i)  $V_{GS(off)}$  and (ii)  $g_m$  at mid-point bias. [(i)  $-5$  V (ii) 3000  $\mu$ S]
6. At a certain point on the transfer characteristics of an *N*-channel JFET, following values are read :  $I_{DSS} = 8.4$  mA,  $V_{GS} = -0.5$  V and  $V_P = -3.0$  V.  
 Calculate (i)  $g_{mo}$  and (ii)  $g_m$  at the point. [(i) 5600  $\mu$ S (ii) 4670  $\mu$ S]
7. For the JFET circuit of Fig. 63.22,  $I_{DSS} = 9$  mA and  $V_P = -3$  V.  
 Find the value of  $R_L$  for setting the value of  $V_{DS}$  at 7 V. [5 K]  
(Hint :  $V_{GS} = -2$  V as  $I_G = 0$ )

 


Fig. 63.21

Fig. 63.22

\* Miller effect occurs only where output is antiphase with input as CS amplifier circuit.



### 63.13. MOSFET or IGFET

It could be further subdivided as follows :

#### (i) Depletion-enhancement MOSFET or DE MOSFET

This MOSFET is so called because it can be operated in both **depletion** mode and **enhancement** mode by changing the polarity of  $V_{GS}$ . When negative gate-to-source voltage is applied, the  $N$ -channel DE MOSFET operates in the depletion mode. However, with positive gate voltage, it operates in the enhancement mode. Since a channel exists between drain and source,  $I_D$  flows even when  $V_{GS} = 0$ . That is why DE MOSFET is known as **normally-ON MOSFET**.

#### (ii) Enhancement-only MOSFET

As its name indicates, this MOSFET operates only in the enhancement mode and has no depletion mode. It works with **large positive** gate voltages only. It differs in construction from the DE MOSFET in that structurally **there exists no channel between the drain and source**. Hence, it does not conduct when  $V_{GS} = 0$ . That is why it is called **normally-OFF** MOSFET.

In a DE MOSFET,  $I_D$  flows even when  $V_{GS} = 0$ . It operates in depletion mode with negative values of  $V_{GS}$ . As  $V_{GS}$  is made more negative,  $I_D$  decreases till it ceases when  $V_{GS} = V_{GS(off)}$ . It works in enhancement mode when  $V_{GS}$  is positive as shown in Fig. 63.24 (b).

In the case of E-only MOSFET,  $I_D$  flows only when  $V_{GS}$  exceeds  $V_{GS(th)}$  as shown in Fig. 63.30 (c).


 


Fig. 63.23

### 63.14. DE MOSFET
 
#### (a) Construction

Like JFET, it has source, gate and drain. However, as shown in Fig. 63.23, its gate is insulated from its conducting channel by an ultra-thin metal-oxide insulating film (usually of silicon dioxide  $\text{SiO}_2$ ). Because of this insulating property, MOSFET is alternatively known as insulated-gate field-



effect transistor (IGFET or IGT). Here also, gate voltage controls drain current but main difference between JFET and MOSFET is that, in the latter case, we can apply **both positive and negative voltages to the gate because it is insulated from the channel**. Moreover, the gate,  $\text{SiO}_2$  insulator and channel form a parallel-plate capacitor. Unlike JFET, a DE MOSFET has only one P-region or N-region called substrate. Normally, it is shorted the **source internally**. Fig. 63.23 shows both P-channel and N-channel DE MOSFETs along with their symbols.

**(b) Working**

**(i) Depletion Mode of N-channel DE MOSFET**

When  $V_{GS} = 0$ , electrons can flow freely from source to drain through the conducting channel which exists between them. When gate is given negative voltage, it **depletes** the N-channel of its

 


Fig. 63.24

electrons by including positive charge in it as shown in Fig. 63.24 (a). Greater the negative voltage on the gate, greater is the reduction in the number of electrons in the channel and, consequently, lesser its conductivity. In fact, too much negative gate voltage called  $V_{GS(off)}$  can cut-off the channel. Hence, with negative gate voltage, a DE MOSFET behaves like a JFET.

For obvious reasons, negative-gate operation of a DE MOSFET is called its depletion mode operation.

**(ii) Enhancement Mode of N-channel DE MOSFET**

The circuit connections are shown in Fig. 63.24 (b). Again, drain current flows from source to drain even with zero gate bias. When positive voltage is applied to the gate, the input gate capacitor is able to create free electrons in the channel which increases  $I_D$ . As seen from the enlarged view of the gate capacitor in Fig. 63.24 (b), free electrons are induced in the channel **by capacitor action**. These electrons are added to those already existing there. This increased number of electrons **increases** or **enhances** the conductivity of the channel. As positive gate voltage is increased, the number of induced electrons is increased, so conductivity of the source-to-drain channel is increased and, consequently, increasing amount of current flows between the terminals. That is why, positive gate operation of a DE MOSFET is known as its **enhancement mode** operation.

Since gate current in both modes is negligibly small, input resistance of a MOSFET is incredibly high varying from  $10^{10} \Omega$  to  $10^{14} \Omega$ . In fact, MOSFET input current is the leakage current of the capacitor unlike the input current for JFET which is the leakage current of a reverse-biased P-N junction.



### 63.15. Schematic Symbols for a DE MOSFET

Schematic symbol of an  $N$ -channel normally-ON or DE MOSFET is shown in Fig. 63.25. The gate looks like a metal plate. The arrow is on the substrate and **towards the  $N$ -channel**. When  $SS$  is connected to an external load, we have a 4-terminal device as shown in Fig. 63.25 (a) but when it is internally shorted to  $S$ , we get a 3-terminal device as shown in Fig. 63.25 (b). Fig. 63.25 (c) shows the symbol for a  $P$ -channel DE MOSFET.

 


Fig. 63.25

### 63.16. Static Characteristics of a DE MOSFET

In Fig. 63.26 are shown the drain current and transfer characteristics of a common-source  $N$ -channel DE MOSFET for  $V_{GS}$  varying from  $+2$  V to  $V_{GS(off)}$ .

 


Fig. 63.26

It acts in the enhancement mode when gate is **positive** with respect to source and in the depletion mode when gate is **negative**. As usual,  $V_{GS(off)}$  represents the gate-source voltage which cuts off the source-to-drain current. The transfer characteristic is shown in Fig. 63.26 (b). For a given  $V_{DS}$ ,  $I_D$  flows even when  $V_{GS} = 0$ . However, keeping  $V_{DS}$  constant, as  $V_{GS}$  is made more negative,  $I_D$  keeps decreasing till it becomes zero at  $V_{GS} = V_{GS(off)}$ . When used in the enhancement mode,  $I_D$  increases as  $V_{DS}$  is increased positively.

**Example 63.9.** For the  $N$ -channel zero-biased DE MOSFET circuit of Fig. 63.27, calculate  $V_{DS}$  if  $I_{DSS} = 10$  mA and  $V_{GS(off)} = -6$  V.

(Electronics-I, Bangalore Univ. 1992)

 


Fig. 63.27

**Solution.** Since  $I_D = I_{DSS} = 10 \text{ mA}$   
 $\therefore V_{DS} = V_{DD} - I_{DSS} R_L$   
 $= 18 - 10 \times 10^{-3} \times 800 = 10 \text{ V}$

### 63.17. Enhancement-only N-Channel MOSFET

This *N*-channel MOSFET (also called NMOS) finds wide application in digital circuitry. As shown in Fig. 63.28 in the NMOS, the *P*-type substrate extends all the way to the metal-oxide layer. Structurally, **there exists no channel between the source and drain**. Hence, an NMOS can never operate with a negative gate voltage because it will induce **positive** charge in the space between the drain and source which will not allow the passage of electrons between the two. Hence, it operates with **positive gate voltage only**.

The normal biasing polarities of this *E*-only MOSFET (both *N*-channel and *P*-channel) are shown in Fig. 63.29. With  $V_{GS} = 0$ ,  $I_D$  is non-existent even when some positive  $V_{DD}$  is applied. It is found that for getting significant amount of drain current, we have to apply sufficiently high positive gate voltage. This voltage is found to produce a thin layer of free electrons very close to the metal-oxide film which stretches all the way from source to drain. The thin layer of *P*-substrate touching the metal-oxide film which provides channel for electrons (and hence acts like *N*-type material) is called ***N*-type inversion layer or virtual *N*-channel** [Fig. 63.29 (a)].

The minimum gate-source voltage which produces this *N*-type inversion layer and hence drain current is called threshold voltage  $V_{GS(th)}$  as shown in Fig. 63.30 (c). When  $V_{GS} < V_{GS(th)}$ ,  $I_D = 0$ . Drain current starts only when  $V_{GS} > V_{GS(th)}$ . For a given  $V_{DS}$ , as  $V_{GS}$  is increased, virtual channel deepens and  $I_D$  increases. The value of  $I_D$  is given by  $I_D = K(V_{GS} - V_{GS(th)})^2$  where  $K$  is a constant which depends on the particular MOSFET. Its value can be determined from the data sheet by taking the specified value of  $I_D$  called  $I_{D(ON)}$  at the given value of  $V_{GS}$  and then substituting the values in the above equation. Fig. 63.30 (a)

 


Fig. 63.28

 


Fig. 63.29

shows the schematic symbol for an *E*-only *N*-channel MOSFET whereas Fig. 63.30 (b) shows its typical drain characteristics. As usual, arrow on the substrate points to the *N*-type material and the vertical line (representing-channel) is broken as a reminder of the normally-OFF condition.



 


Fig. 63.30

A P-channel E-only MOSFET (PMOS) is constructed like NEMS except that all the *P*- and *N*-regions are interchanged. It operates with **negative** gate voltage only.

Differentiating the above-given drain current equation with respect to  $V_{GS}$ , we get

$$\frac{dI_D}{dV_{GS}} = g_m = 2K (V_{GS} - V_{GS(th)})$$

### Transfer Characteristics

It is shown in Fig. 63.30 (c),  $I_D$  flows only when  $V_{GS}$  exceeds threshold voltage  $V_{GS(th)}$ . This MOSFET does not have an  $I_{DSS}$  parameter as do the JFET and DE MOSFET.

### 63.18. Biasing E-only MOSFET

As stated earlier, enhancement-only MOSFET must have a  $V_{GS}$  greater than  $V_{GS(th)}$ . Fig. 63.31 shows two methods of biasing an *N*-channel E-MOSFET. In either case, the purpose is to make the gate voltage more positive than the source by an amount exceeding  $V_{GS(th)}$ . Fig. 63.31 (a) shows drain-feedback bias whereas Fig. 63.31 (b) shows voltage-divider bias.

Considering the circuit of Fig. 63.31 (b), we have

$$V_{GS} = V_2 = V_{DD} \frac{R_2}{R_1 + R_2}$$

and  $V_{DS} = V_{DD} - I_D R_L$

where  $I_D = K(V_{GS} - V_{GS(th)})^2$ .

 


Fig. 63.31

**Example 63.10.** The data sheet of the E-MOSFET shown in Fig. 63.32 gives  $I_{D(ON)} = 4 \text{ mA}$  at  $V_{GS} = 10 \text{ V}$  and  $V_{GS(th)} = 5 \text{ V}$ . Calculate  $V_{GS}$  and  $V_{DS}$  for the circuit.

(Applied Electronics, Punjab Univ. 1991)

**Solution.**  $V_{GS} = V_2 = 25 \times (9/15) = 15 \text{ V}$

Let us now find the value of  $K$ .

$$K = \frac{I_{D(ON)}}{(V_{GS} - V_{GS(th)})^2} = \frac{4}{(10 - 5)^2} = 0.16 \text{ mA/V}^2$$

 


Fig. 63.32

Value of  $I_D$  for  $V_{GS}=15\text{ V}$  is given by

$$I_D = K (V_{GS} - V_{GS(th)})^2 = 0.16 (15 - 5)^2 = 16\text{ mA}$$

$$\text{Now, } V_{DS} = V_{DD} - I_D R_L = 25 - 16 \times 1 = \mathbf{9\text{ V}}$$

**Example 63.11.** An N-channel E-MOSFET has the following parameters:

$$I_{D(ON)} = 4\text{ mA at } V_{GS} = 10\text{ V and } V_{GS(th)} = 5\text{ V}$$

Calculate its drain current for  $V_{GS} = 8\text{ V}$ .

**Solution.**  $K = \frac{I_{D(ON)}}{(V_{GS} - V_{GS(th)})^2} = \frac{4\text{ mA}}{(10\text{ V} - 5\text{ V})^2} = 0.16\text{ mA/V}^2$

Now, using this value of  $K$ ,  $I_D$  can be found thus :

$$I_D = K (V_{GS} - V_{GS(th)})^2 = 0.16 (8 - 5)^2 = \mathbf{1.44\text{ mA}}$$

### 63.19. FET Amplifiers

We will consider the DE MOSFET and E-MOSFET separately.

 


Fig. 63.33

#### (i) DE MOSFET Amplifier

Fig. 63.33 (a) shows a zero-biased N-channel DE MOSFET with an ac source capacitively-coupled to its gate. Since gate is at 0 volt dc and source is at ground,  $V_{GS} = 0$ . Fig. 63.33 (b) shows the transfer characteristic.

The input ac signal voltage  $V_i$  causes  $V_{GS}$  to swing above and below its zero value thus producing a swing in  $I_D$  as shown in Fig. 63.33 (b). The negative swing in  $V_{GS}$  produces depletion mode and  $I_D$

 


Fig. 63.34

is decreased. A positive swing in  $V_{GS}$  produces enhancement mode so that  $I_D$  is increased. This leads to a large swing in drop across  $R_L$  and can be taken out via  $C_2$  as  $V_o$ .

### (ii) E-MOSFET Amplifier

In Fig. 63.34 (a) is shown a voltage-divider biased  $N$ -channel E-MOSFET having an ac signal source coupled to its gate. The gate is biased with a positive voltage such that  $V_{GS}$  exceeds  $V_{GS(th)}$ .

As shown in Fig. 63.34 (b), the signal voltage produces a swing in  $V_{GS}$  below and above its  $Q$ -point value. This, in turn, causes a swing in  $I_D$  and hence in  $I_D R_L$  which gives rise to no.

**Example 63.12.** The  $N$ -channel E-MOSFET used in the common-source amplifier of Fig. 63.35 has the following parameters :

$I_{D(ON)} = 4 \text{ mA}$  at  $V_{DS} = 10 \text{ V}$ ,  $V_{GS(th)} = 4 \text{ V}$  and  $g_m = 5000 \mu\text{S}$ .

Calculate  $V_{GS}$ ,  $I_D$ ,  $V_{GS}$  and  $v_o$ . (Elect. and Electronic Engg., Annamalai Univ. 1992)

**Solution.**  $V_{GS} = V_{DD} \frac{R_2}{R_1 + R_2} = 16 \times \frac{30}{80} = 6 \text{ V}$

Now,  $K = \frac{I_{D(ON)}}{(V_{GS} - V_{GS(th)})^2} = \frac{4}{(10 - 5)^2}$   
 $= 0.16 \text{ mA/V}^2$

$\therefore I_D = K(V_{GS} - V_{GS(th)})^2 = 0.16(6 - 4)^2$   
 $= 0.64 \text{ mA}$

$\therefore V_{DS} = V_{DD} - I_D R_L = 16 - 0.64 \times 5 = 12.8 \text{ V}$

Now,  $A_v = g_m(r_d \parallel R_L) \cong g_m R_L$   
 $= 5000 \times 10^{-6} \times 5 \times 10^3 = 25$

$\therefore V_o = A_v v_i = 25 \times 100 = 2500 \text{ mV} = 2.5 \text{ V}$

 


Fig. 63.35

**Example 63.13.** The parameters of the enhancement-only NMOS shown in Fig. 63.36 are  $V_{GS(th)} = 2 \text{ V}$  and  $K = 2 \times 10^{-4} \text{ A/V}^2$ . Calculate the values of  $I_D$  and  $V_{DS}$ .

**Solution.** Since drain is directly returned to gate,  $V_{GS} = V_{DS}$ . As seen from the figure

 


Fig. 63.36

$$\begin{aligned} V_{DS} &= V_{DD} - I_D R_L = 12 - 5 \times 10^3 I_D \\ \therefore I_D &= (12 - V_{DS}) / 5 \times 10^3 \text{ A} \\ \text{Now, } I_D &= K(V_{GS} - V_{GS(th)})^2 = K(V_{DS} - 2)^2 \\ \text{or } \frac{12 - V_{DS}}{5 \times 10^3} &= 2 \times 10^{-4} (V_{DS} - 2)^2 \text{ or } V_{DS}^2 - 3V_{DS} - 8 = 0 \\ \therefore V_{DS} &= \frac{3 \pm \sqrt{9 + 32}}{2} = \frac{3 \pm \sqrt{41}}{2} = 4.7 \text{ V} \\ \therefore I_D &= (12 - 4.7) / 5 \times 10^3 = 1.5 \text{ mA} \end{aligned}$$

In Fig. 63.36 (b), since gate has been directly returned to ground,  $V_{GS} = 0$ . Hence,  $I_D = 0$ , because  $V_{GS} \ll V_{GS(th)}$ . With no current,  $V_{DS} = V_{DD} = 12 \text{ V}$ .

**Example 63.14.** A MOSFET has a drain resistance,  $R_L$  of  $44 \text{ k}\Omega$  and operates at  $20 \text{ kHz}$ . Calculate the voltage gain of this device as a single stage amplifier. The MOSFET parameters are :  $g_m = 1.6 \text{ mA/V}$ ,  $r_d = 100 \text{ k}\Omega$ ,  $C_{gs} = 3.0 \text{ pF}$ ,  $C_{ds} = 1.0 \text{ pF}$  and  $C_{gd} = 2.8 \text{ pF}$ .

(U.P.S.C. Engg. Services, 1996)

**Solution.**  $A_v = g_m(r_d \parallel R_L)$   
 $= 1.6 \times 10^{-3} (100 \times 10^3 \parallel 44 \times 10^3)$   
 $= 1.6 \times 10^{-3} \times 30.56 \times 10^3$   
 $= 48.9$





### 63.20. FET Applications

FETs can be used in almost every application in which bipolar transistors can be used. However, they have certain applications which are exclusive to them :

1. As input amplifiers in oscilloscopes, electronic voltmeters and other measuring and testing equipment because their high  $r_{in}$  *reduces loading effect to the minimum.*
2. In logic circuits where it is kept OFF when there is zero input while it is turned ON with very little power input.
3. For mixer operation of *FM* and *TV* receivers.
4. As voltage-variable resistor (*VVR*) in operational amplifiers and tone controls etc.
5. Large-scale integration (*LSI*) and computer memories because of very small size.

### 63.21. MOSFET Handling

MOSFETs require very careful handling particularly when *out of circuit*. In circuit, a MOSFET is as rugged as any other solid-state device of similar construction and size.

It is essential not to permit any stray or static voltage on the gate otherwise the ultra-thin  $\text{SiO}_2$  layer between the channel and the gate will get ruptured. Since gate-channel junction looks like a capacitor with extremely high resistance, it requires only a few electrons to produce a high voltage across it. Even *picking up a MOSFET by its leads can destroy it*. Generally, grounding rings are used to short all leads of a MOSFET for avoiding any voltage build up between them. These grounding or shorting rings are removed only after MOSFET is securely wired into the circuit. Sometimes, conducting foam is applied between the leads instead of using shorting rings. As shown in Fig. 13.37, some MOSFETs have back-to-back Zener diodes internally formed to protect them against stray voltages.

 


Fig. 63.37

### Tutorial Problems No. 63.2

1. For a certain DE MOSFET,  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -8 \text{ V}$ . Calculate  $I_D$  when  $V_{GS}$  is (i)  $-4 \text{ V}$  and (ii)  $+4 \text{ V}$ . [ (i) **2.5 mA** (ii) **22.5 mA** ]
2. The data sheet of a certain zero-biased DE MOSFET gives  $I_{DSS} = 15 \text{ mA}$  and  $V_{GS(off)} = 5 \text{ V}$ . What is the value of drain current ? [**15 mA**]
3. A certain *E*-only *N*-channel MOSFET has the following parameters :  
 $I_{D(on)} = 4 \text{ mA}$  at  $V_{GS} = 8 \text{ V}$  and  $V_{GS(th)} = 2 \text{ V}$   
 Calculate  $I_D$  for  $V_{GS} = 6 \text{ V}$  [**1.78 mA**]

 


Fig. 63.38

4. The parameters of the *E*-only, *N*-channel MOSFET shown in Fig. 63.38 (a) are :  $V_{GS(th)} = 2 \text{ V}$  and  $K = 0.3 \text{ mA/V}^2$ . Determine the values of  $I_D$  and  $V_{DS}$ . If the gate is connected as shown in Fig. 63.38 (b), what will be the new values of  $I_D$  and  $V_{DS}$ ? **[(i) 2.07 mA (ii) 4.63 V ; 0 A, 15 V]**
5. The data sheet for the *E*-only *N*-channel MOSFET of Fig. 63.38 (c) gives  $I_{D(on)} = 3 \text{ mA}$  at  $V_{GS} = 10 \text{ V}$  and  $V_{GS(th)} = 5 \text{ V}$ . Calculate the values of  $V_{GS}$  and  $V_{DS}$ . **[14.4 V ; 13.4 V]**
6. The amplifier circuit of Fig. 63.38 (d) used an *E*-only *N*-channel MOSFET having the following parameters :  $I_{D(on)} = 5 \text{ mA}$  at  $V_{GS} = 10 \text{ V}$ ,  $V_{GS(th)} = 4 \text{ V}$ ,  $g_m = 5500 \mu\text{S}$ . Calculate  $V_{GS}$ ,  $I_D$ ,  $V_{DS}$  and  $v_o$ . **[6 V ; 0.556 mA ; 12.2 V ; 0.825 V]**
7. A field-effect transistor has a small-signal equivalent circuit with input resistance =  $1000 \text{ M}\Omega$ , forward transfer conductance =  $4 \text{ mS}$  and output conductance =  $100 \mu\text{S}$  when at the operating point,  $V_{DS} = +4 \text{ V}$ ,  $I_D = 2 \text{ mA}$ ,  $V_{GS} = -2 \text{ V}$ .  
Draw the circuit that you would use for a single-stage voltage amplifier. Describe the use and specify the value of as many components as possible if a  $30 \text{ V}$  supply was available.  
What voltage gain would you expect when the output was unloaded? Give reasons which might account for not getting this gain exactly.  
**[Drain load =  $12 \text{ k}\Omega$ , Source Bias Resistor =  $1 \text{ k}\Omega$ , - 21.8]**
8. A field-effect transistor is used as a voltage amplifier and with a load resistor of  $40 \text{ k}\Omega$ , a gain of 40 is obtained. If the load resistance is halved, the voltage gain drops to 30. Calculate the output resistance and the mutual conductance of the transistor.  
Briefly compare the advantages and limitations of the field-effect transistor with the bipolar transistor. **[20 k $\Omega$ , 3 mS]**

### OBJECTIVE TESTS – 63

- A FET consists of a
  - source
  - drain
  - gate
  - all of the above.
- FETs have similar properties to
  - PNP transistors
  - NPN transistors
  - thermonic valves
  - unijunction transistors.
- For small values of drain-to-source voltage, JFET behaves like a
  - resistor
  - constant-current source
  - constant-voltage source
  - negative resistance
- In a JFET, the *primary* control on drain current is exerted by
  - channel resistance
  - size of depletion regions
  - voltage drop across channel
  - gate reverse bias.
- After  $V_{DS}$  reaches pinch-off value  $V_p$  in a JFET, drain current  $I_D$  becomes
  - zero
  - low
  - saturated
  - reversed.
- In a JFET, as external bias applied to the gate is increased
  - channel resistance is decreased
  - drain current is increased
  - pinch-off voltage is reached at lower values of  $I_D$ .
  - size of depletion regions is reduced.
- In a JFET, drain current is maximum when  $V_{GS}$  is
  - zero
  - negative
  - positive
  - equal to  $V_p$
- The voltage gain of a given common-source JFET amplifier depends on its
  - input impedance
  - amplification factor
  - dynamic drain resistance
  - drain load resistance.
- A JFET has the disadvantage of
  - being noisy
  - having small gain-bandwidth product
  - possessing positive temperature coefficient
  - having low input impedance.
- A JFET can be cut-off with the help of
  - $V_{GS}$
  - $V_{DS}$
  - $V_{DG}$
  - $V_{DD}$



11. The drain source voltage at which drain current becomes nearly constant is called  
 (a) barrier voltage  
 (b) breakdown voltage  
 (c) pick-off voltage  
 (d) pinch-off voltage
12. The transconductance ' $g_m$ ' of a JFET is equal to  
 (a)  $-\frac{2I_{DSC}}{V_p}$   
 (b)  $\frac{2}{|V_p|} \sqrt{I_{DSS} I_D}$   
 (c)  $-\frac{2I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p}\right)$   
 (d)  $\frac{I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p}\right)$
13. An FET source follower circuit has of 2 millimho and of 50 k  $\Omega$ . If the source resistance  $R_s$  is 1k  $\Omega$ , the output resistance of the amplifier will be  
 (a) 330  $\Omega$  (b) 450  $\Omega$   
 (c) 500  $\Omega$  (d) 1 k  $\Omega$
14. A DE MOSFET differs from a JFET in the sense that it has no  
 (a) channel (b) gate  
 (c) P-N junctions (d) substrate.
15. For the operation of enhancement only N-channel MOSFET, value of gate voltage has to be  
 (a) high positive (b) high negative  
 (c) low positive (d) zero.
16. The extremely high input impedance of a MOSFET is primarily due to the  
 (a) absence of its channel  
 (b) negative gate-source voltage  
 (c) depletion of current carriers  
 (d) extremely small leakage current of its gate capacitor
17. The main factor which makes a MOSFET likely to break down during normal handling is its  
 (a) very low gate capacitance  
 (b) high leakage current  
 (c) high input resistance  
 (d) both (a) and (c).
18. The main factor which differentiates a DE MOSFET from an E-only MOSFET is the absence of  
 (a) insulated gate (b) electrons  
 (c) channel (d) P-N junctions.
19. The polarity of  $V_{GS}$  for E-only MOSFET is  
 (a) positive  
 (b) negative  
 (c) zero  
 (d) depends on P-or N-channel.
20. A transconductance amplifier has  
 (a) high input impedance and low output impedance  
 (b) low input impedance and high output impedance  
 (c) high input and output impedances  
 (d) low input and output impedances
21. The threshold voltage of an n-channel enhancement mode MOSFET is 0.5 V, when the device is biased at a gate voltage of 3V, pinch-off would occur at a drain voltage of  
 (a) 1.5 V (b) 2.5 V  
 (c) 3.5 V (d) 4.5 V
22. The zero gate bias channel resistance of a junction field-effect transistor is 750  $\Omega$  and the pinch-off voltage is 3V. For a gate bias of 1.5 V and very low drain voltage, the device would behave as a resistance of  
 (a) 320  $\Omega$  (b) 816  $\Omega$   
 (c) 1000  $\Omega$  (d) 1270  $\Omega$
23. A MOSFET rated for 15 A, carries a periodic current as shown in Fig. 63.39. the ON state resistance of the MOSFET is 0.15  $\Omega$ . The average ON state loss in the MOSFET is

 


Fig. 63.39

- (a) 33.8 W (b) 15.0 W  
 (c) 7.5 W (d) 3.8 W

## ANSWERS

1. (d) 2. (b) 3. (a) 4. (d) 5. (c) 6. (c) 7. (a) 8. (d) 9. (b) 10. (a) 11. (d)  
 12. (c) 13. c 14. (c) 15. (a) 16. (d). 17. (d) 18. (c) 19. (d) 20. (a) 21. (c) 22. (b)  
 23. (c)

## ROUGH WORK