

# Lecture 5a

## Digital Logic - Basic Logic Gates

Chintan Kr Mandal



# Outlines

In this series of lectures we are going to discuss

- in detail the various basic Gates [1]
- designing of boolean logic circuits using the basic gates
- minimizing the boolean expressions

# The Basic Digital Gates !!



"MY WIFE'S IDEA OF THE FOUR BASIC FOOD GROUPS IS  
CANNED, FROZEN, FREEZE-DRIED AND CARRY-OUT."

# Digital Logic Gates

# The Gate


The term **Gate** is used to describe a circuit that performs a basic logic operation.

*Input(s) are on the left, and the output is on the right of each gate (symbol)*

## Digital Logic Gates
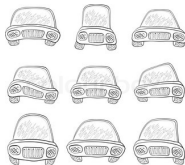
### Dual Inline Packages (DIP)

- The Inverter
- The AND Gate
- The OR Gate
- The NAND Gate
- The NOR Gate
- The Exclusive-OR Gate
- The Exclusive-NOR Gate



## The Inverter



## Inverters (NOT Gate)

- The inverter (NOT Gate/circuit) performs the operation called *inversion* or *complementation*.
- The inverter changes one logic level to the opposite level.
- In terms of bits, it changes a **1 to a 0** and a **0 to a 1**

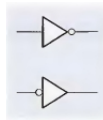


Figure: Distinctive shape symbols with negation indicators

## The Negation and Polarity Indicators

- The negation indicator is a “bubble” (○) that indicates **inversion** or *complementation* when it appears on the input or output of any logic element.

Generally *inputs are on the left of a logic symbol and the output is on the right*

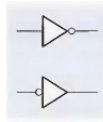


Figure: Distinctive shape symbols with negation indicators

## The Negation and Polarity Indicators


- \* When appearing on the input, the bubble means that a 0 is the *active* or *asserted* input state, and the input is called an **active-LOW** input.
- \* When appearing on the output, the bubble means that a 0 is the *active* or *asserted* output state, and the input is called an **active-HIGH** input.

## Inverter Truth Table

When a HIGH level is applied to an inverter input, a LOW level will appear on its output and vice-versa

INPUT (I)	OUTPUT (O)
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

## Inverter Operation

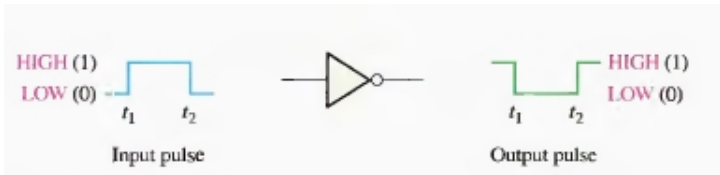

**Figure:** Inverter operation with a pulse input;  $t_1$  and  $t_2$  indicate the corresponding points on the input and output pulse waveform


## Logic Expression for an Inverter

In **Boolean Algebra**, the **complement** of a variable is designated by a bar over the letter.

$$X = \bar{A}$$

where

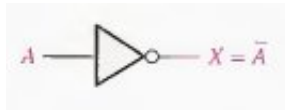- A is the input variable
- X is the output variable



- 1 If A is 1 then X is 0
- 2 If A is 0 then X is 1

## Example 1

A waveform is applied to an inverter.



Figure: Waveform is applied to input

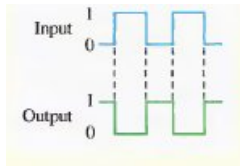


Figure: The output waveform

## Example 2

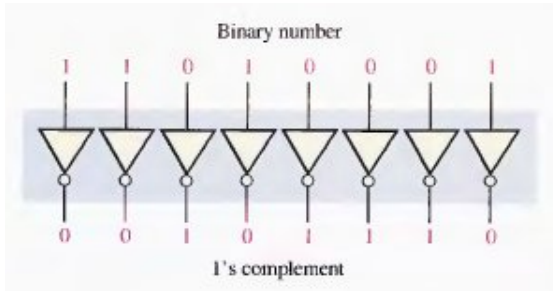


Figure: 1's Complement



## The AND Gate

# The AND Gate


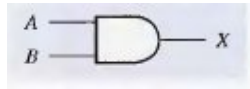


Figure: Symbol of AND Gate

- The AND gate is composed of two or more inputs and a single output.
- An AND gate can have any number of inputs greater than one.

**Note** For a 2-input AND gate, output **X** is **HIGH** only when inputs **A** and **B** are **HIGH**; **X** is **LOW** when either **A** or **B** is **LOW**, or when both **A** and **B** are **LOW**.


## Logic Levels of AND Gate

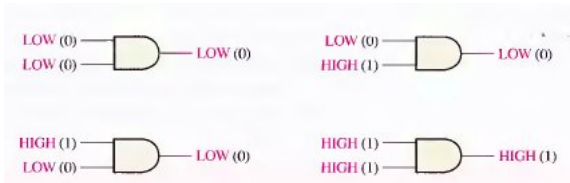

A	B	o/p
LOW (0)	LOW (0)	LOW (0)
LOW (0)	HIGH (1)	LOW (0)
HIGH (1)	LOW (0)	LOW (0)
HIGH (1)	HIGH (1)	HIGH (1)


All possible logic levels for a 2-input AND gate.

## Operation with Waveform Inputs

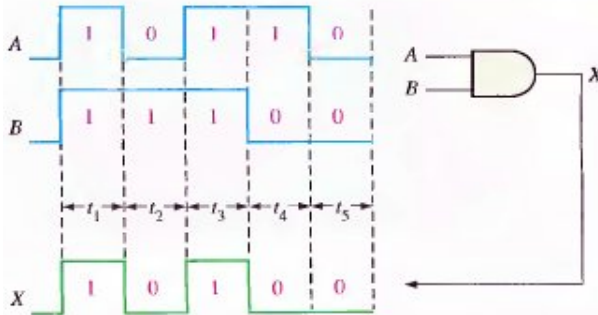


**Figure:** AND gate operation with a timing diagram showing input and output relationships.
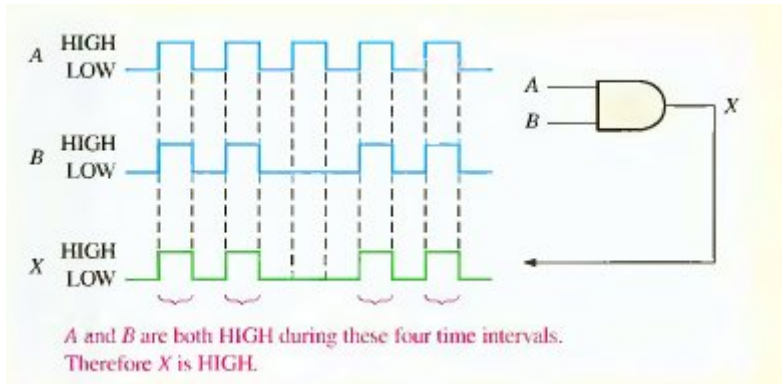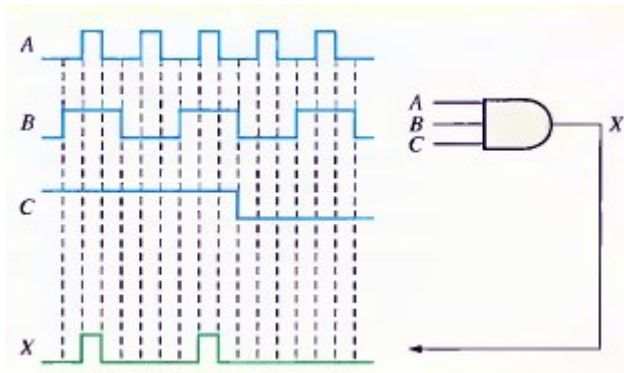
## Example with Waveform Inputs



## Example with Waveform Inputs



## Logic Expressions for an AND Gate

The logical AND function of two variables is represented mathematically either by placing a dot between the two variables, as

$$A.B$$

or as

$$AB$$

## Example

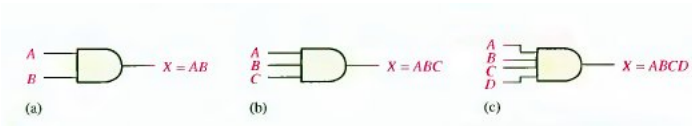


Figure: AND Logic gate symbol with multiple inputs

A	B	$X=A.B$
0	0	0
0	1	0
1	0	0
1	1	1

Table: Truth Table of 2-Input AND Gate



## Example - Three Input AND Gate

A	B	C	X=ABC
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table: Truth Table of 3-Input AND Gate

The total number of input combinations for  $n$  inputs in  $N = 2^n$

E.g. For  $n = 3$ , the total number of input combinations are  
 $N = 2^3 = 8$ .

## Application

The AND Gate follows the same basic rules of **Boolean multiplication**

$$0.0 = 0$$

$$0.1 = 0$$

$$1.0 = 0$$

$$1.1 = 1$$

## Application

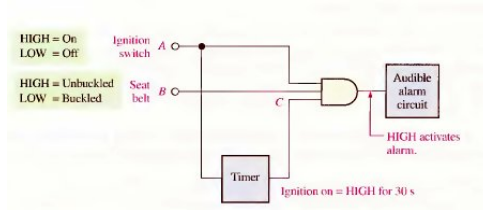


Figure: A Seat Belt Alarm System

- When the ignition is turned on, a timer is started that produces a HIGH on input C for 30sec
- If the ignition is *on* **AND** seat belt is *unbuckeled* **AND** timer is *running* - the output of AND gate is HIGH and the timer is **ON**

## The OR Gate

## The OR Gate


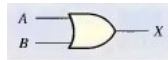


Figure: OR Gate

- The OR gate is composed of two or more inputs and a single output.
- An OR gate can have any number of inputs greater than one.

**Note** For a 2-input OR gate, output **X** is **HIGH** when either input **A** or input **B** is **HIGH**, or when both **A** and **B** are **HIGH**; **X** is **LOW** only when both **A** and **B** are **LOW**.


## Logic Levels of OR Gate

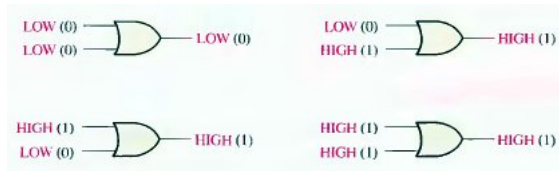

A	B	o/p
LOW (0)	LOW (0)	LOW (0)
LOW (0)	HIGH (1)	HIGH (1)
HIGH (1)	LOW (0)	HIGH (1)
HIGH (1)	HIGH (1)	HIGH (1)


All possible logic levels for a 2-input OR gate.

## Operation with Waveform Inputs

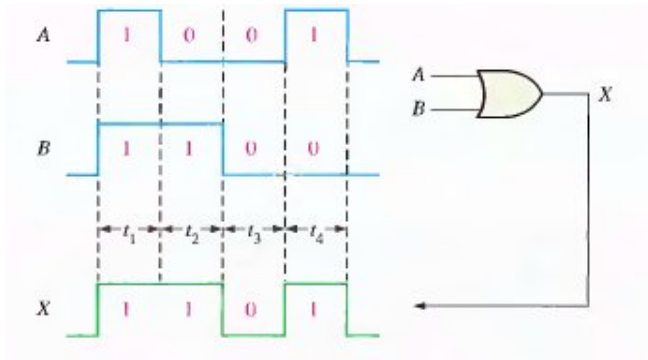


**Figure:** OR gate operation with a timing diagram showing input and output relationships.

## Example with Waveform Inputs

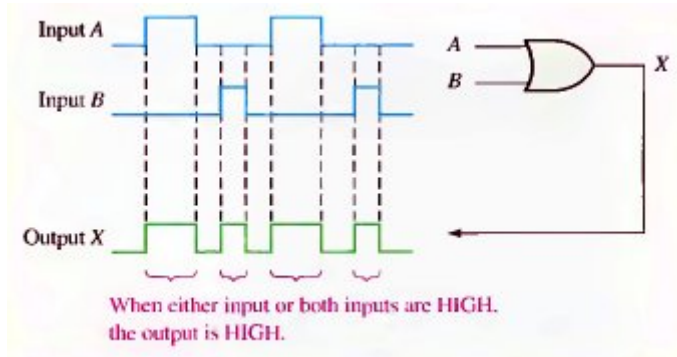



## Example with Waveform Inputs

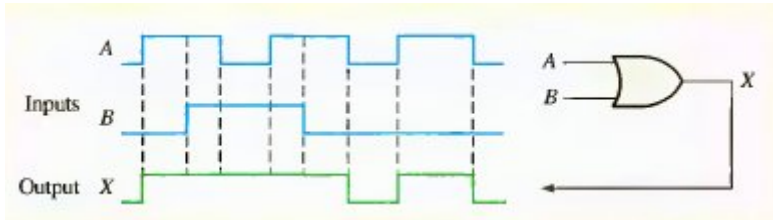

## Logic Expressions for an OR Gate

The logical OR function of two variables is represented mathematically as

$$A + B$$

## Example

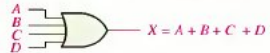
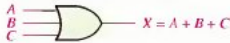


Figure: OR Logic gate symbol with multiple inputs

A	B	$X = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Table: Truth Table of 2-Input OR Gate

## Example - Three Input OR Gate

A	B	C	$X = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table: Truth Table of 3-Input OR Gate

The total number of input combinations for  $n$  inputs in  $N = 2^n$

E.g. For  $n = 3$ , the total number of input combinations are  
 $N = 2^3 = 8$ .

# Application

The OR Gate has the same basic rules of **Boolean additon**

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

## Application

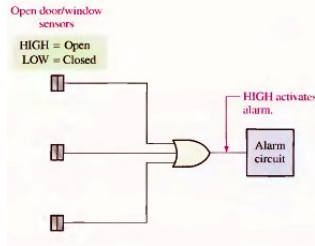


Figure: An Open Window-Door System

- This system could be used for one room in a home-a room with two windows and a door having magnetic switches.
- It activates when one of the windows or the door is opened.

## The NAND Gate

## The NAND Gate

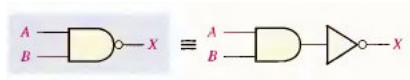



Figure: NAND Gate

- The NAND gate is composed of two or more inputs and a single output.
- An NAND gate can have any number of inputs greater than one.

**Note** For a 2-input NAND gate, output **X** is **LOW** only when inputs **A** and **B** are **HIGH**; **X** is **HIGH** when either **A** or **B** is **LOW**, or when both **A** and **B** are **LOW**.




## Logic Levels of NAND Gate

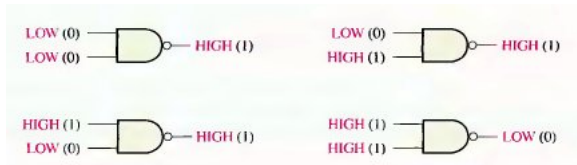

A	B	o/p
LOW (0)	LOW (0)	HIGH (1)
LOW (0)	HIGH (1)	HIGH (1)
HIGH (1)	LOW (0)	HIGH (1)
HIGH (1)	HIGH (1)	LOW (0)

All possible logic levels for a 2-input NAND gate.

## Operation with Waveform Inputs

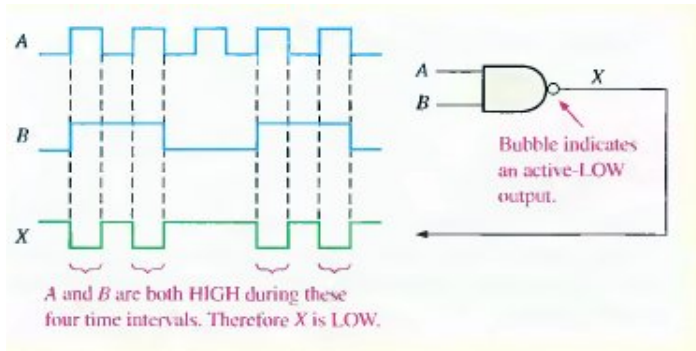


**Figure:** NAND gate operation with a timing diagram showing input and output relationships.

## Logic Expressions for an NAND Gate


The logical AND function of two variables is represented mathematically as

$$X = \overline{AB}$$

## Example with Waveform Inputs

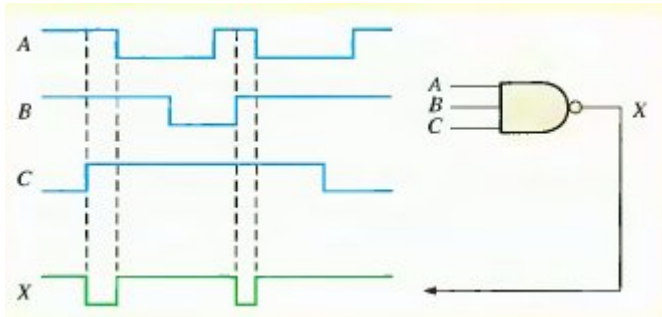

## Negative-OR Equivalent Operation of a NAND Gate

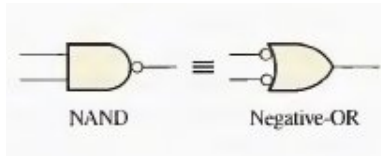


**Figure:** Standard symbols representing the two equivalent operation of a NAND gate.
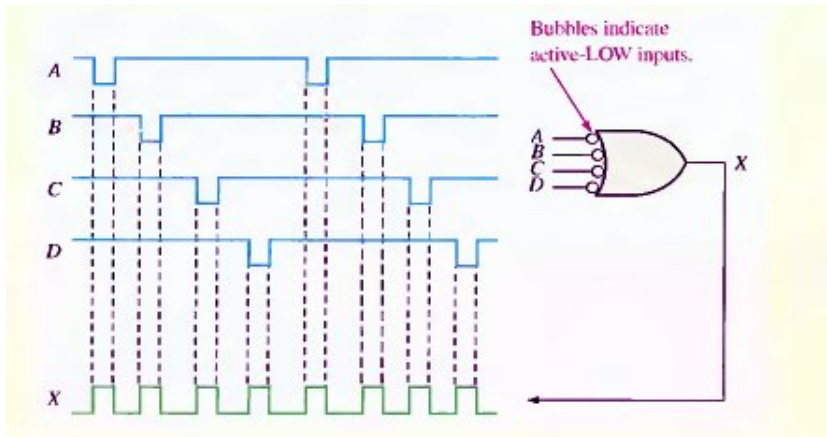
### The De' Morgan Boolean Law (for NAND Gates)

$$\overline{AB} = \overline{A} + \overline{B}$$

## Example with Waveform Inputs



## Truth Table for 2-input NAND Gate

A	B	$X = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

Table: Truth Table of 2-Input NAND Gate

## Example - Three Input NAND Gate

A	B	C	$X = \overline{ABC}$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table: Truth Table of 3-Input NAND Gate



## Application

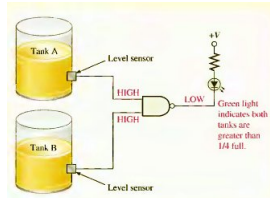


Figure: A Water tankIndicator

- If tank A and tank B are above one-quarter full, the LED is on.

## The NOR Gate

## The NOR Gate


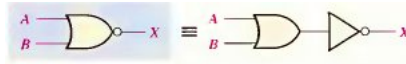


Figure: NOR Gate

- The NOR gate is composed of two or more inputs and a single output.
- An NOR gate can have any number of inputs greater than one.

**Note** For a 2-input NOR gate, output X is LOW when either input A or input B is HIGH, or when both A and B are HIGH; X is HIGH only when both A and B are LOW.


## Logic Levels of NOR Gate

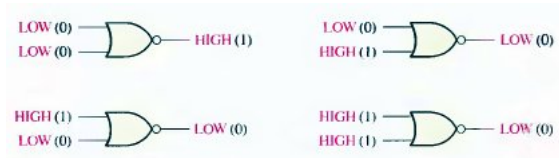

A	B	o/p
LOW (0)	LOW (0)	HIGH (1)
LOW (0)	HIGH (1)	LOW (0)
HIGH (1)	LOW (0)	LOW (0)
HIGH (1)	HIGH (1)	LOW (0)

All possible logic levels for a 2-input NOR gate.

## Operation with Waveform Inputs

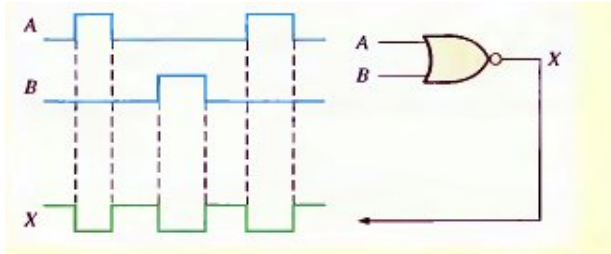


**Figure:** NOR gate operation with a timing diagram showing input and output relationships.

## Logic Expressions for an NOR Gate


The logical NOR function of two variables is represented mathematically as

$$X = \overline{A + B}$$

## Example with Waveform Inputs

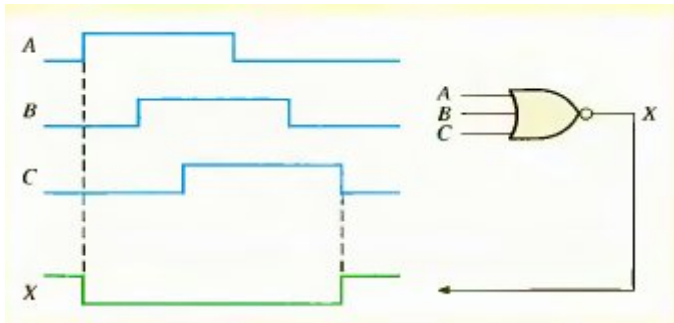

## Negative-AND Equivalent Operation of a NOR Gate

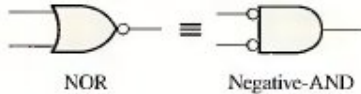

**Figure:** Standard symbols representing the two equivalent operation of a NOR gate.

The De' Morgan Boolean Law (for NOR Gates)

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



## Truth Table for 2-input NOR Gate

A	B	$X = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0


Table: Truth Table of 2-Input NOR Gate

## Example - Three Input NOR Gate

A	B	C	$X = \overline{A + B + C}$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Table: Truth Table of 3-Input NOR Gate

## Application

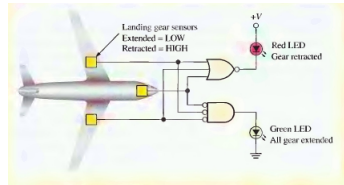

**Figure:** An Aircraft Landing Gears Status Indicator

- A green LED display turns on if all three gears are properly extended when the "gear down" switch has been activated in preparation for landing.
- A red LED display turns on if any of the gears fail to extend properly prior to landing.

**Note** Implement two circuits for the above

## The Exclusive-OR Gate

## The Exclusive-OR (XOR) Gate


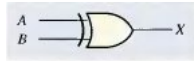


Figure: Exclusive-OR (XOR) Gate

- The XOR gate is composed of two or more inputs and a single output.
- An XOR gate can have any number of inputs greater than one.

**Note** For an exclusive-OR gate. output **X** is **HIGH** when input **A** is **LOW** and input **B** is **HIGH**, or when input **A** is **HIGH** and input **B** is **LOW**: **X** is **LOW** when **A** and **B** are both **HIGH** or both **LOW**.


## Logic Levels of XOR Gate

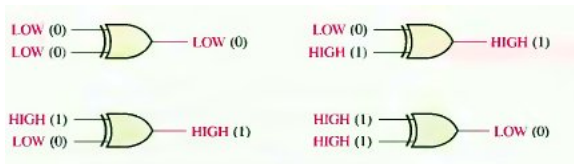

A	B	o/p
LOW (0)	LOW (0)	LOW (0)
LOW (0)	HIGH (1)	HIGH (1)
HIGH (1)	LOW (0)	HIGH (1)
HIGH (1)	HIGH (1)	LOW (0)

All possible logic levels for a 2-input XOR gate.

## Operation with Waveform Inputs

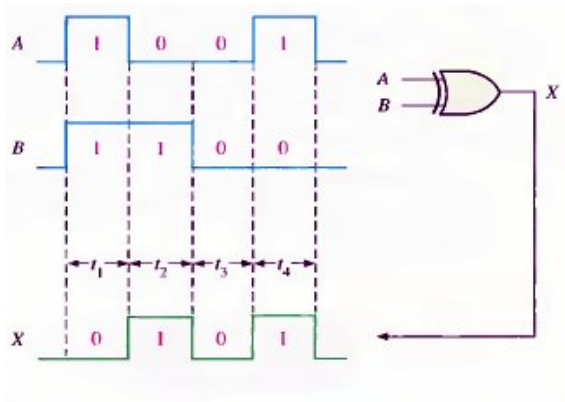

**Figure:** XOR gate operation with a timing diagram showing input and output relationships.

## Logic Expressions for an XOR Gate

### Logic Expression

The logical XOR function of two variables is represented mathematically as

$$X = A \oplus B$$

### Equivalent AND-OR XOR Gates

$$A \oplus B = \bar{A}.B + A.\bar{B}$$



## Truth Table for 2-input XOR Gate

A	B	$X = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Table: Truth Table of 2-Input XOR Gate

## Application

Input bits		Output (sum)
A	B	$\Sigma$
0	0	0
0	1	1
1	0	1
1	1	0 (without 1 carry)


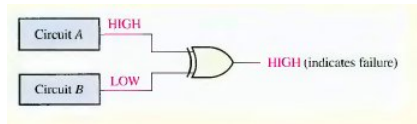


Figure: XOR as Binary Adder without Carry

## Application



**Figure:** Circuit Failure Status Indicator

- A certain system contains two identical circuits operating in parallel.
- As long as both are operating properly, the outputs of both circuits are always the same.
- If one of the circuits fails, the outputs will be at opposite levels at some time.

## The Exclusive-NOR Gate

## The Exclusive-NOR (XNOR) Gate

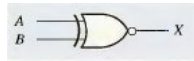


Figure: Exclusive-OR (XOR) Gate

- The XNOR gate is composed of two or more inputs and a single output.
- An XNOR gate can have any number of inputs greater than one.

**Note** For an exclusive-NOR gate, output **X** is **LOW** when input **A** is **LOW** and input **B** is **HIGH**, or when **A** is **HIGH** and **B** is **LOW**; **X** is **HIGH** when **A** and **B** are both **HIGH** or both **LOW**.


## Logic Levels of XNOR Gate



A	B	o/p
LOW (0)	LOW (0)	HIGH (1)
LOW (0)	HIGH (1)	LOW (0)
HIGH (1)	LOW (0)	LOW (0)
HIGH (1)	HIGH (1)	HIGH (1)

All possible logic levels for a 2-input XNOR gate.

## Operation with Waveform Inputs

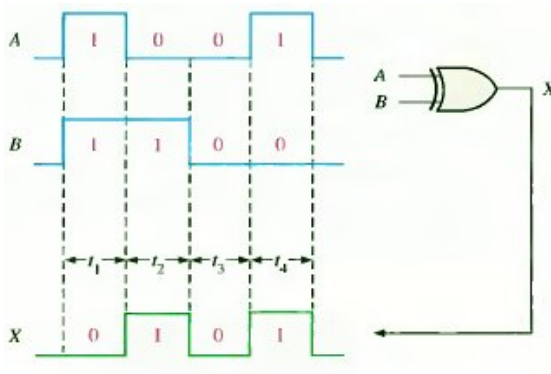

**Figure:** XNOR gate operation with a timing diagram showing input and output relationships.

## Logic Expressions for an XNOR Gate

### Logic Expression

The logical XNOR function of two variables is represented mathematically as

$$X = \overline{A \oplus B}$$

### Equivalent AND-OR XOR Gates

$$\overline{A \oplus B} = \overline{A}.\overline{B} + A.B$$



## Truth Table for 2-input XNOR Gate


A	B	$X = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

Table: Truth Table of 2-Input XNOR Gate

## Digital Logic Gates
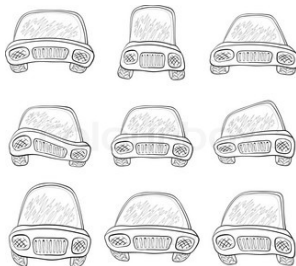
### Dual Inline Packages (DIP)

The Inverter  
The AND Gate  
The OR Gate  
The NAND Gate  
The NOR Gate  
The Exclusive-OR Gate  
The Exclusive-NOR Gate



# Dual Inline Packages (DIP)

## Digital Integrated Circuits


# Digital Integrated Circuits

- A monolithic **integrated circuit (IC)** is an electronic circuit that is constructed entirely on a single chip of silicon
- All the components that make up the circuit - transistors, diodes, resistors and capacitors - are an integral part of that single chip
- Fixed-function logic and programmable logic are two categories of digital ICs.
- In fixed-function logic, the logic functions are set by the manufacturer and cannot be altered.

# IC Packages

- Integrated Circuit (IC) packages are classified according to the way they are mounted on printed circuit (PC) boards as either *through-hole* mounted or *surface* mounted
- The through-hole type packages have pins (leads) that are inserted through holes in the PC board.
- The pins can be soldered to conductors on the opposite side,
- The most common type of through-hole package is the *dual in-line package* (**DIP**)

# Dual Inline Packages (DIP)

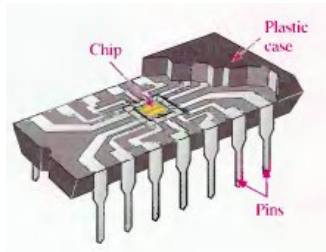

# Pin Numbering

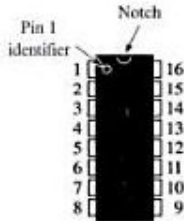


Figure: Pin Numbering for DIP



## Digital IC Packages

## Inverters (IC 7404)

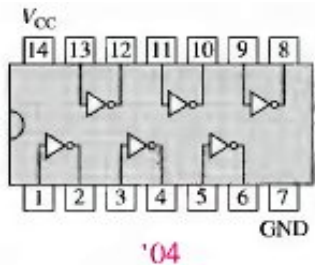


Figure: IC 7404 - Inverter DIP

## 2-Input AND (IC 7408)

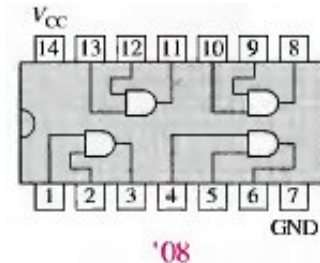


Figure: IC 7408 - 2-Input AND DIP

## 3-Input AND (IC 7411)

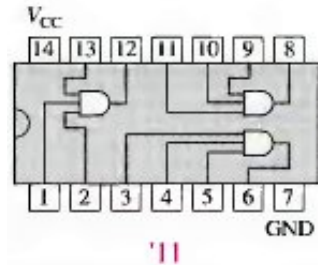


Figure: IC 7411 - 3-Input AND DIP

## 4-Input AND (IC 7421)

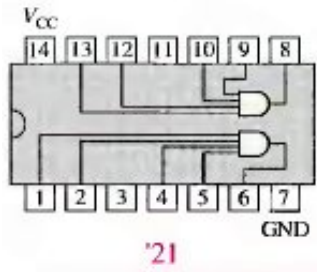


Figure: IC 7421 - 4-Input AND DIP

## 2-Input OR (IC 7432)

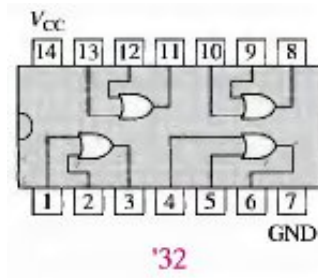


Figure: IC 7432 - 2-Input OR DIP

## 2-Input NAND (IC 7400)

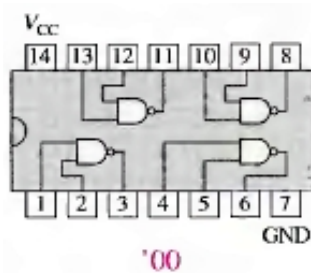


Figure: IC 7400 - 2-Input NAND DIP

## 3-Input NAND (IC 7410)

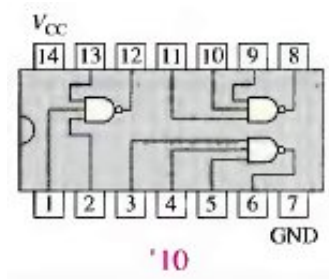


Figure: IC 7410 - 3-Input NAND DIP



## 4-Input NAND (IC 7420)

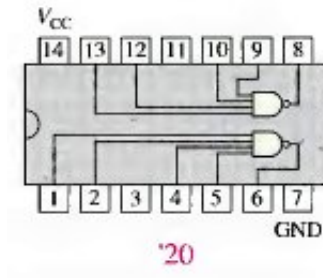


Figure: IC 7420 - 4-Input NAND DIP

## 8-Input NAND (IC 7430)

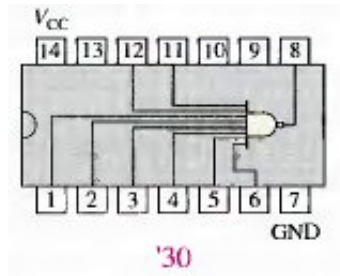


Figure: IC 7430 - 8-Input NAND DIP

## 2-Input NOR (IC 7402)

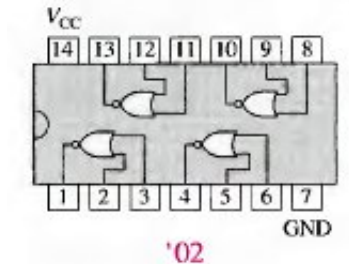


Figure: IC 7402 - 2-Input NOR DIP

## 3-Input NOR (IC 7427)

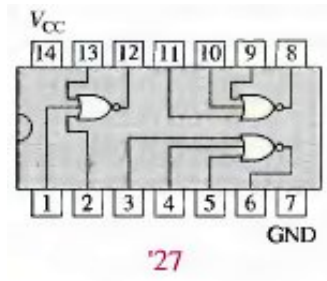


Figure: IC 7427 - 3-Input NOR DIP

## 2-Input XOR (IC 7486)

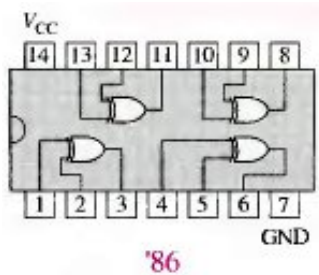


Figure: IC 7486 - 2-Input XOR DIP

# References

- [1] Thomas L. Floyd.  
*Digital Fundamentals, 8th edition.*  
Pearson Education Inc., 2003.

QUESTIONS !!!